

# Electricity Review

Electrical Concept	Symbol	Unit
VOLTAGE	V	V (VOLTS)
CURRENT	I	A (AMPS)
RESISTANCE	R	$\Omega$ (OHMS)
POWER	P	W (WATT)

Ohm's Law:

$$V = IR$$

VOLTAGE = CURRENT  $\times$  RESISTANCE


Power:

$$P = VI = I^2R$$

power = voltage  $\times$  current = current squared  $\times$  resistance
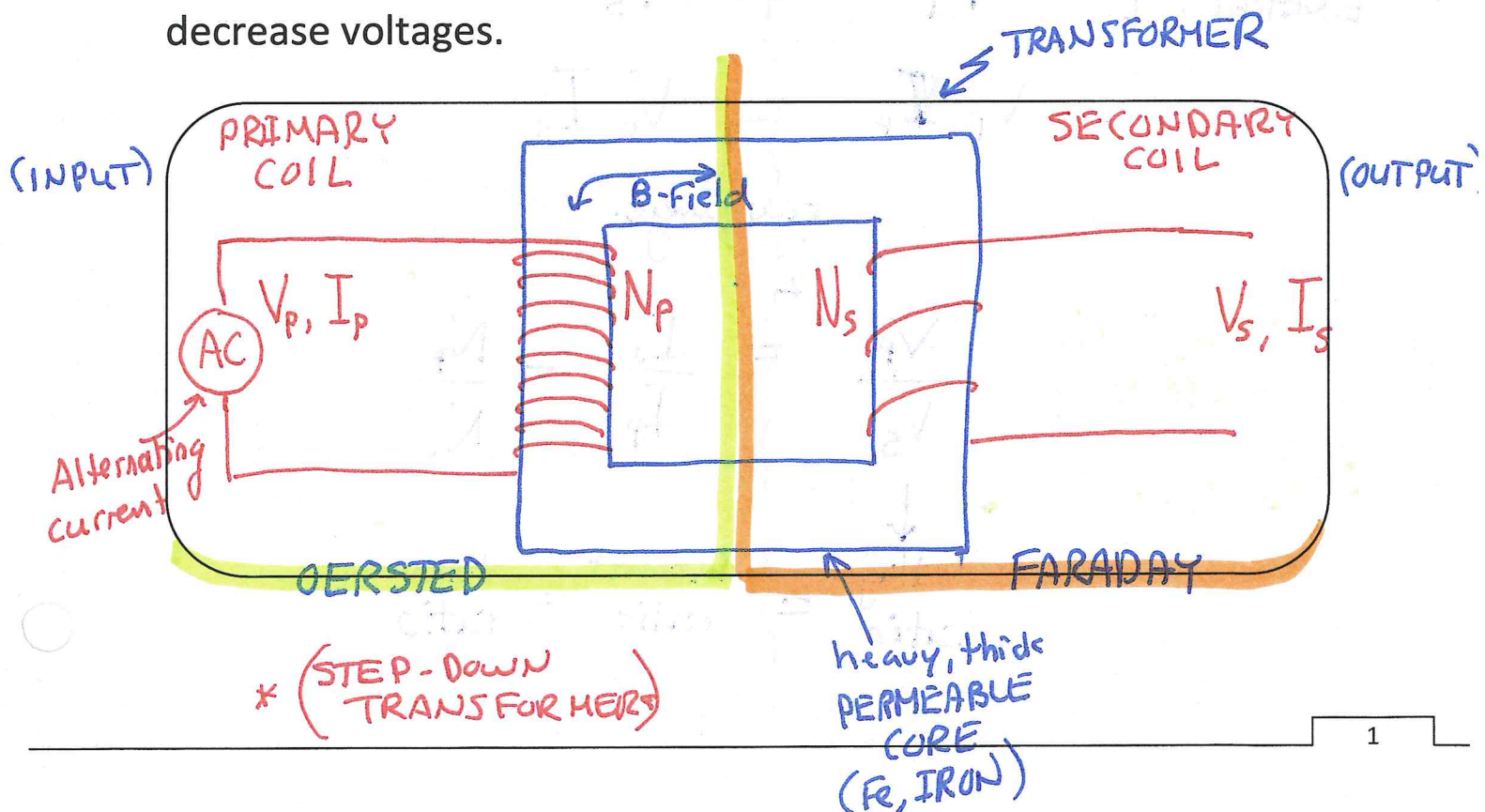
## Transformers

Transformers are used to change (transform) voltages from one value to another value. They are used to either increase or decrease voltages.



**Principle Explanation:**

- The alternating current (AC) in the primary coil produces a changing magnetic field around that coil

**[Oersted's Principle]**

- The changing magnetic field around the primary coil induces a current in the secondary coil

**[Faraday's Law]**

**\*\* if the coils have different number of turns in the coils the voltage will be either increased or decreased.**

**Mathematically:**

Energy cannot be created or destroyed. So the energy and hence the power in each of the coils must be equal.

PRIMARY COIL      SECONDARY COIL

CONSERVATION OF ENERGY {  $P_p = P_s$

$V_p I_p = V_s I_s$

rearrange.

$$\frac{V_p}{V_s} = \frac{I_s}{I_p} = \frac{N_p}{N_s}$$

voltage ratio = current ratio = turn ratio

**TRANSFER EQUATION**

# Transformer Examples

Name: \_\_\_\_\_

TEACHER

Date: \_\_\_\_\_

2013

1. A transformer is made to convert  $20\text{ V AC}$  to a higher voltage. The current in the primary side was found to be  $6\text{ A}$  and on the secondary side it is  $2\text{ A}$ .

a) Calculate the secondary voltage as well as the secondary number of coils if there are 50 primary coils.

- STEP-UP TRANSFORMER -

$$V_p = 20\text{V}$$

$$V_s = ?$$

$$I_p = 6\text{A}$$

$$I_s = 2\text{A}$$

$$N_p = 50$$

$$N_s = ?$$

$$\frac{V_p}{V_s} = \frac{I_s}{I_p} = \frac{N_p}{N_s}$$

$$\frac{20}{V_s} = \frac{2}{6} = \frac{50}{N_s}$$

$$V_s = \frac{20 \times 6}{2}$$

$$N_s = \frac{50 \times 6}{2}$$

$$V_s = 60\text{V}$$

$$N_s = 150$$

STEP-UP  $\Rightarrow V_s > V_p$  and  $I_s < I_p$

STEP-DOWN  $\Rightarrow V_s < V_p$  and  $I_s > I_p$

POWER MUST BE THE SAME!

$\therefore V_s$  is  $60\text{V}$  and  $N_s$  is  $150$  based on the current ratio.

- b) Calculate the power on both sides as well.

$$P_p = P_s$$

$$V_p I_p = V_s I_s$$

$$(20)(6) = (60)(2)$$

$$120\text{W} = 120\text{W} \quad \checkmark$$

THE SAME!

$$I_p^2 R_p = I_s^2 R_s$$



$$P_p = I_p^2 R_p$$

OR

$$P_s = I_s^2 R_s$$

$$120 \text{ W} = (6)^2 R_p$$

$$120 \text{ W} = (2)^2 R_s$$

$$3.3 \Omega = R_p$$

primary resistance.

$$30 \Omega = R_s$$

secondary resistance