

Transformer Example

Name: _____ Date: _____

1. A transformer is made to convert 20 V AC to a higher voltage. The current in the primary side was found to be 6 A and on the secondary side it is 2 A.
 - a) Calculate the secondary voltage as well as the secondary number of coils if there are 50 primary coils.

- b) Calculate the power on both sides as well.

SPH3U – Electricity & Magnetism

- c) Calculate the resistance, R , in each of the coils.